

Chapter9 Theory and Applications of Transmission Lines

Application: Signal Transmission

Models


Electromagnetic theory

General method


Very complicate

Lump-element model


Applied to transmission line only

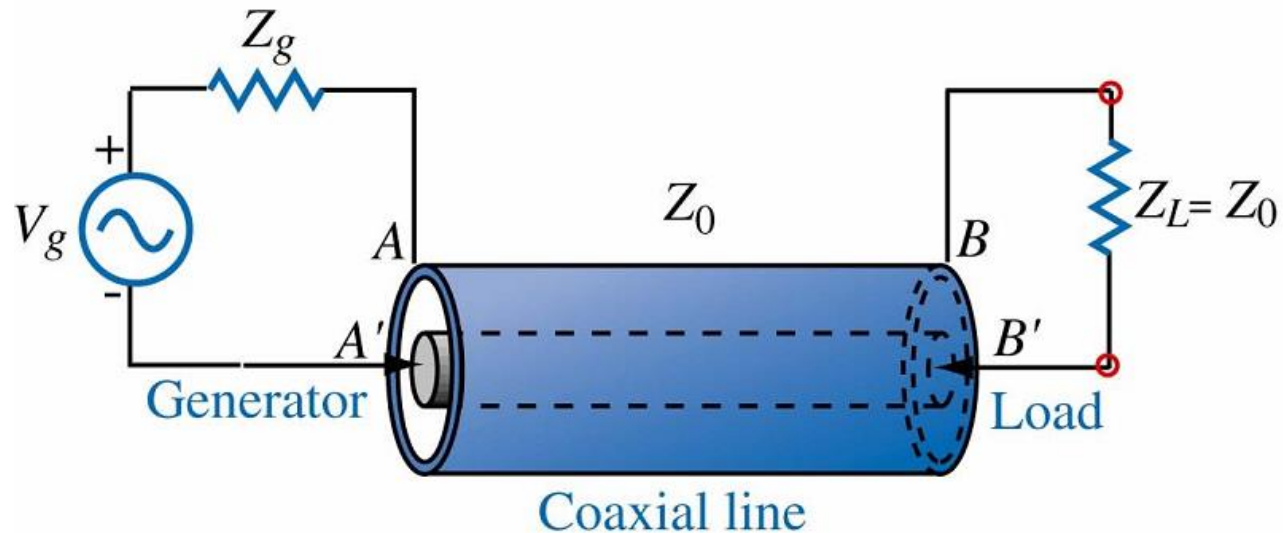


Common types of transmission lines

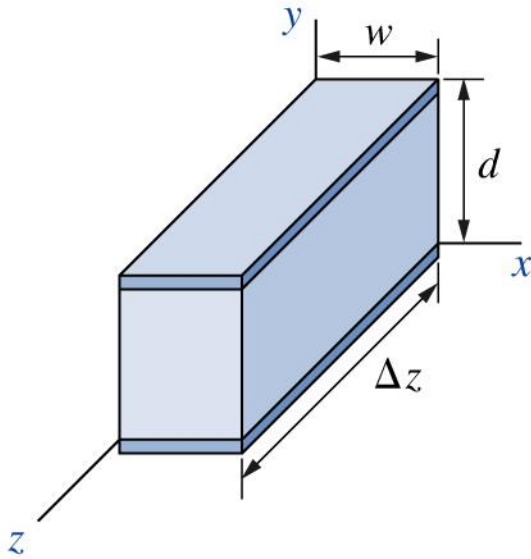

Parallel-plate
transmission line

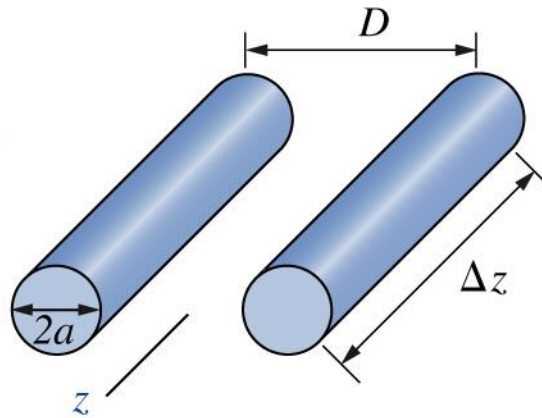

Two-wire (twin-lead)
transmission line

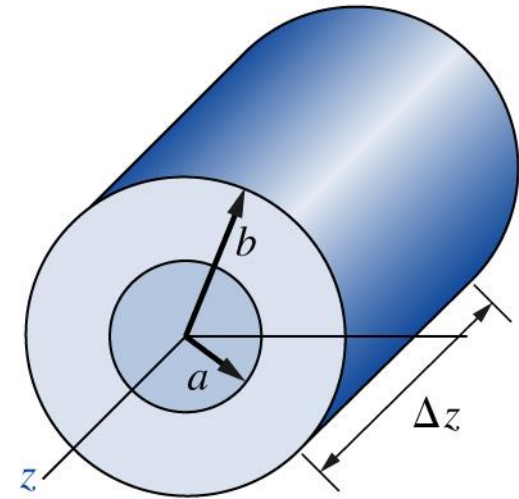


Coaxial
transmission line

Each structure (including the twin lead) may have a dielectric between two conductors used to keep the separation between the metallic elements constant, so that the electrical properties would be constant.


Microstrip line




MICROSTRIP TRANSMISSION LINE

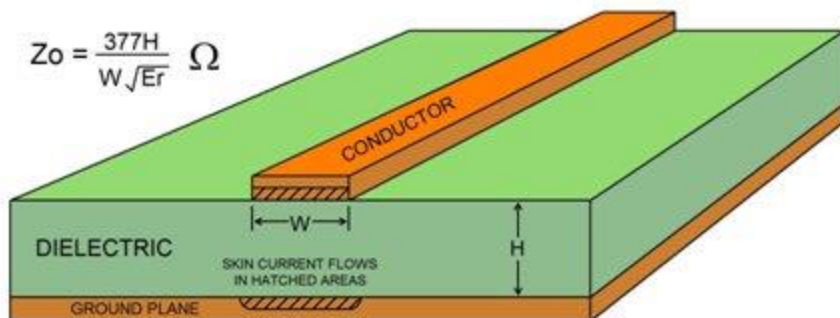


Twin lead

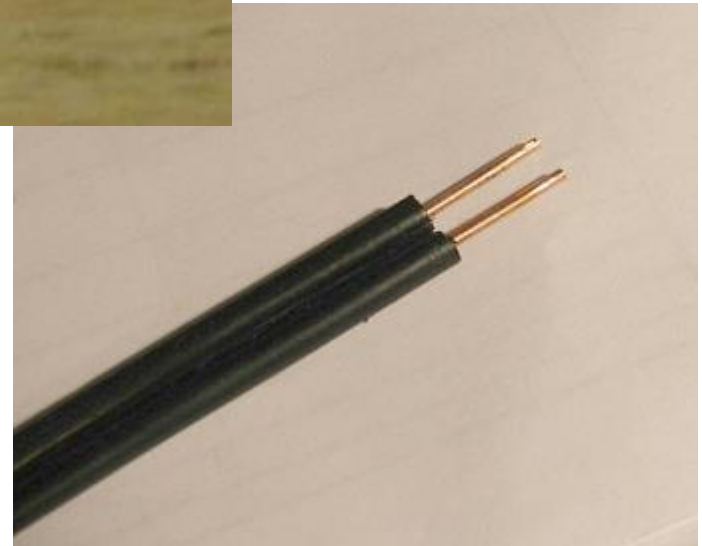

Coaxial cable

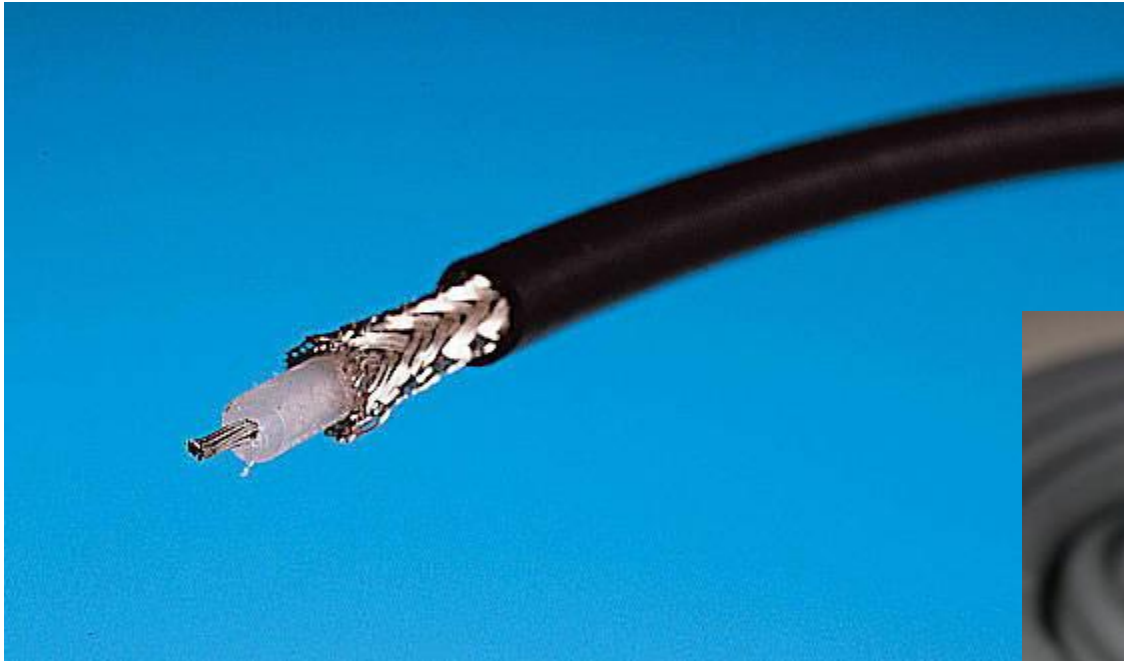

9-2 Parallel-Plate Transmission Line

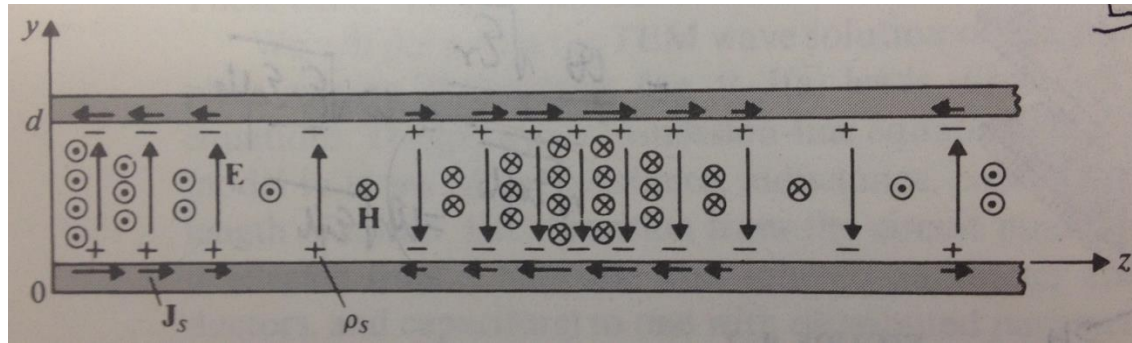

$$\nabla^2 \mathbf{E} - \frac{1}{c^2} \frac{\partial^2 \mathbf{E}}{\partial t^2} = 0 \quad \text{since } \mathbf{E} \propto e^{i\omega t} \rightarrow \nabla^2 \mathbf{E} + \frac{\omega^2}{c^2} \mathbf{E} = 0 \quad (\nabla^2 \mathbf{E} + k_0^2 \mathbf{E} = 0)$$

Assume it's a plane wave propagate in the z with polarization in y direction.

$$\frac{d^2}{dz^2} E_y + k_0^2 E_y = 0 \rightarrow \mathbf{E} = \hat{y} \tilde{E}_0 e^{-ik_0 z + i\omega t}$$

$$\mathbf{H} = -\hat{x} \frac{1}{\sqrt{\frac{\mu}{\epsilon}}} \tilde{E}_0 e^{-ikz + i\omega t} = H_x \hat{x}$$


9-2 Parallel-Plate Transmission Line

Crossing the boundary from dielectric medium to the perfect conduction plates:

$$\nabla \times \vec{E} = -\frac{\partial \vec{B}}{\partial t} \quad \& \quad \nabla \times \vec{B} = \mu\epsilon \frac{\partial \vec{E}}{\partial t}$$

$$\rightarrow \nabla \times \vec{E} = -i\omega\mu\vec{H} \quad \& \quad \nabla \times \vec{H} = i\omega\epsilon\vec{E}$$
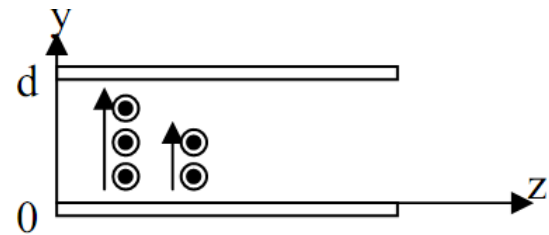
$$\mathbf{E} = \hat{y}\tilde{E}_y(z,t), \quad \mathbf{H} = \hat{x}\tilde{H}_x(z,t) \quad (\vec{E} \rightarrow V, \vec{H} \rightarrow \sigma \rightarrow I)$$



basic differential equations

$$\begin{vmatrix} \hat{i} & \hat{j} & \hat{k} \\ \frac{\partial}{\partial x} & \frac{\partial}{\partial y} & \frac{\partial}{\partial z} \\ 0 & E_y & 0 \end{vmatrix} = -i\omega\mu H_x \rightarrow \frac{dE_y}{dz} = i\omega\mu H_x \quad \& \quad \frac{dH_x}{dz} = i\omega\epsilon E_y$$

9-2 Parallel-Plate Transmission Line

$$\int_0^d \frac{dE_y}{dz} dy = i\omega\mu \int_0^d H_x dy \quad \rightarrow \quad -\frac{dV(z)}{dz} = i\omega LI(z)$$

$L = \mu \frac{d}{w}$ is the inductance per unit length

$$\int_0^w \frac{dH_x}{dz} dx = i\omega\varepsilon \int_0^w E_y dx \quad \rightarrow \quad -\frac{dI(z)}{dz} = i\omega CV(z)$$

$C = \varepsilon \frac{w}{d}$ is the capacitance per unit length

9-2 Parallel-Plate Transmission Line

$$\frac{d^2 V(z)}{dz^2} = -\omega^2 LC V(z) \qquad V(z) = V_0 e^{-ikz}$$

$$\frac{d^2 I(z)}{dz^2} = -\omega^2 LI(z) \qquad I(z) = I_0 e^{-ikz}$$

impedance

$$Z_0 = \frac{V(z)}{I(z)} = \frac{V_0}{I_0} = \frac{\omega L I_0}{k I_0} = \sqrt{\frac{L}{C}} = \sqrt{\frac{\mu d / w}{\epsilon w / d}} = \frac{d}{w} \sqrt{\frac{\mu}{\epsilon}}$$

velocity of propagation
along the line

$$v = \frac{\omega}{k} = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{(\mu d / w)(\epsilon w / d)}} = \frac{1}{\sqrt{\mu \epsilon}}$$

9-2 Parallel-Plate Transmission Line

Dielectric medium between two conductors having a permittivity and a conductivity



Conductance C

The two conductors have a very large but finite conductivity



Resistance R

Distributed Parameters of Parallel-Plate Transmission Line (Width = w , Separation = d)

Parameter	Formula	Unit
R	$\frac{2}{w} \sqrt{\frac{\pi f \mu_c}{\sigma_c}}$	Ω/m
L	$\mu \frac{d}{w}$	H/m
G	$\sigma \frac{w}{d}$	S/m
C	$\epsilon \frac{w}{d}$	F/m

conductor


dielectric

Coaxial transmission line

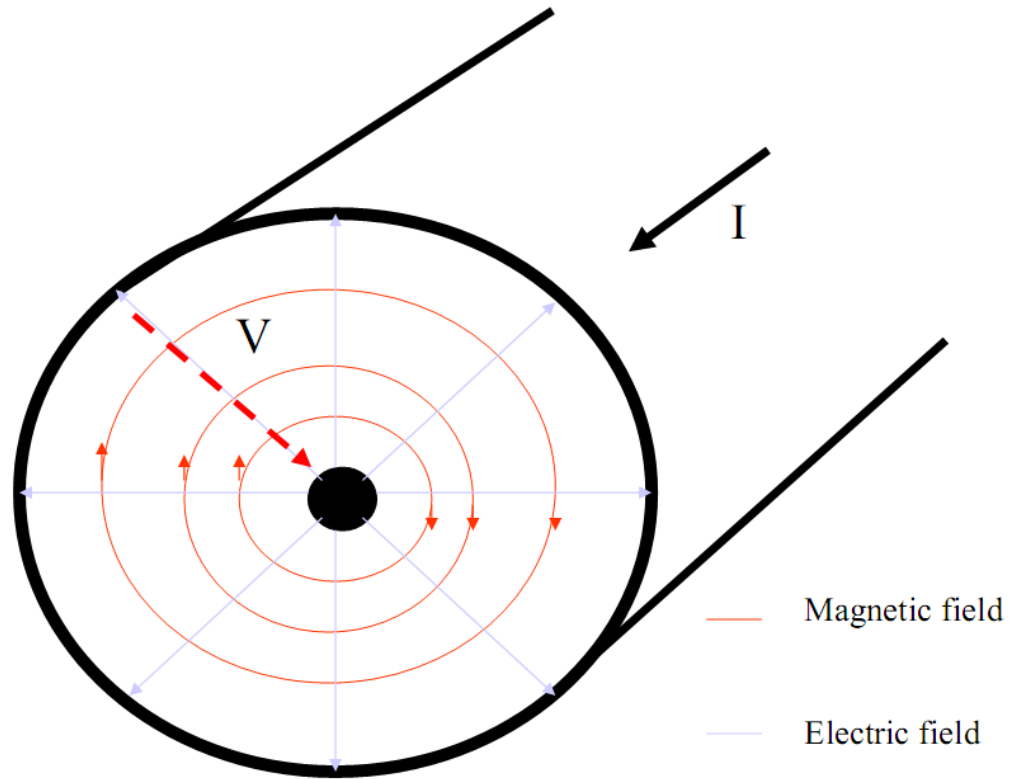Example: E,H,V,I

$$V = -\int_b^a \mathbf{E} \cdot d\mathbf{r}$$


$$I = \oint_l \mathbf{H} \cdot d\mathbf{l}$$




Cross-section of a coaxial cable showing the electric and magnetic fields

Coaxial transmission line

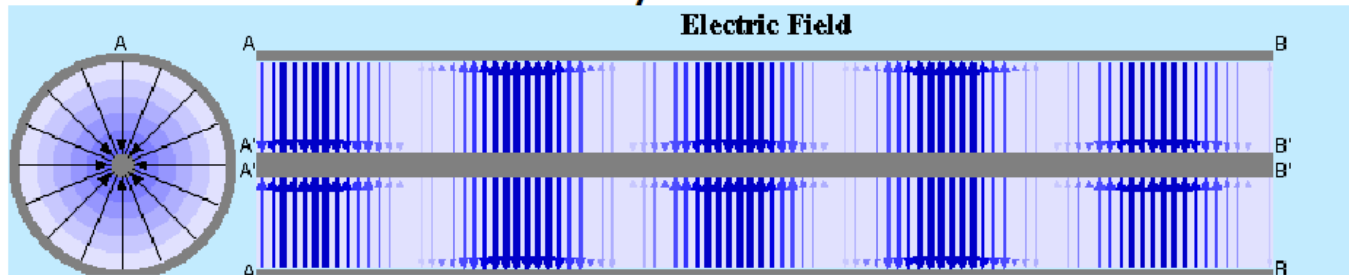
D2.1A Electric field intensity inside a coaxial cable



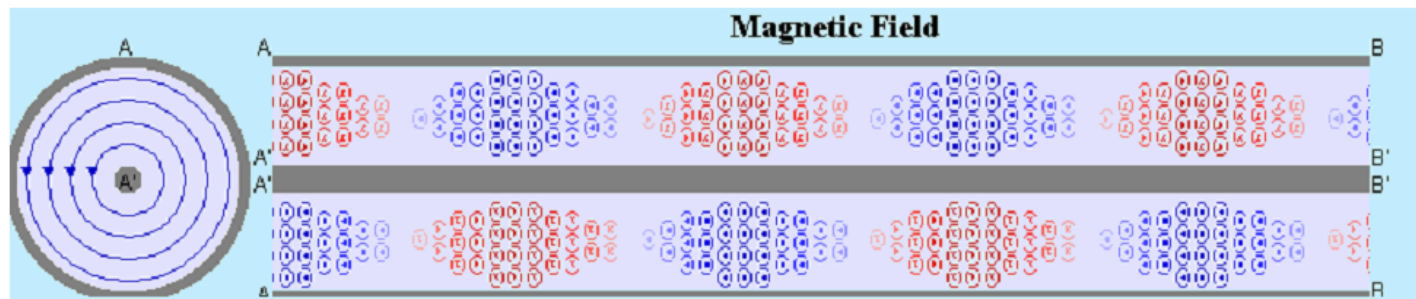D2.3A Magnetic field inside a coaxial cable



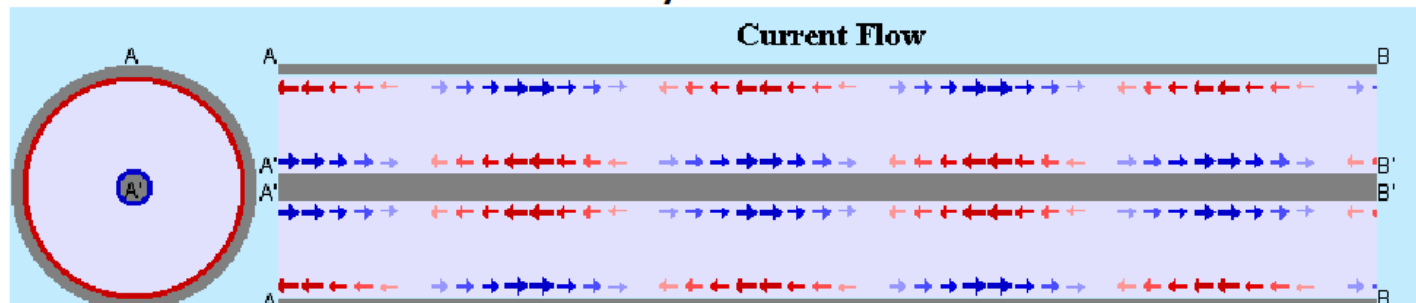D2.4A Electric current density inside a coaxial cable




9-3 General Transmission-line equations

Lumped-element model

Small section of a transmission line (length = Δz)

represented by an equivalent circuit

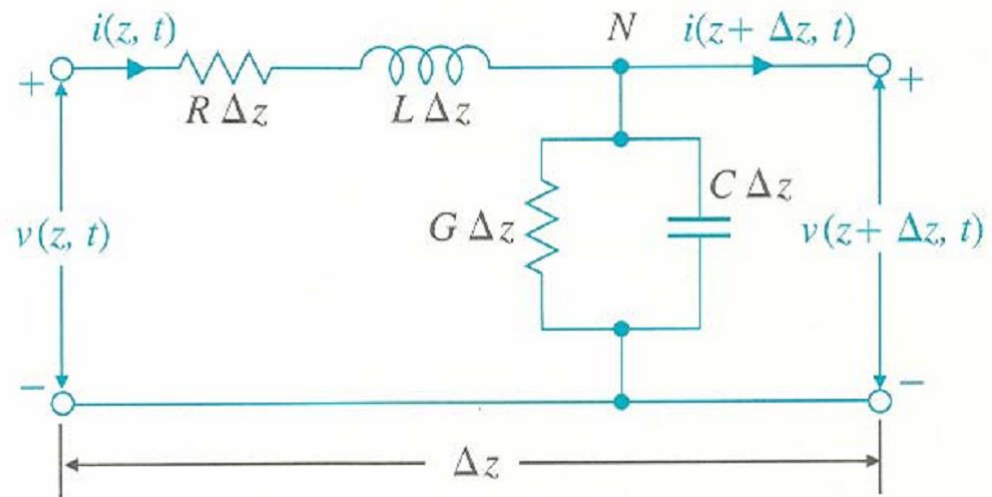

R : Resistance of both conductors per unit length (Ω/m)


L : Inductance of both conductors per unit length (H/m)

G : Conductance of the insulation medium per unit length (S/m)

C : Capacitance of the two conductors per unit length (F/m)

9-3 General Transmission-line equations

1. Applying Kirchhoff's voltage law

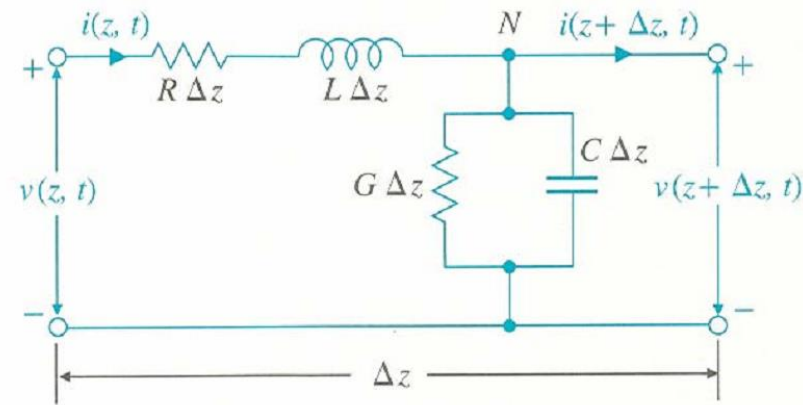


$$\begin{aligned}
 v(z, t) &= v_R + v_L + v(z + \Delta z, t) \\
 &= [R \Delta z] i(z, t) + [L \Delta z] \frac{\partial i(z, t)}{\partial t} + v(z + \Delta z, t) \\
 \Rightarrow \frac{v(z + \Delta z, t) - v(z, t)}{\Delta z} &= -R i(z, t) - L \frac{\partial i(z, t)}{\partial t}
 \end{aligned}$$

at node N

$$\begin{aligned}
 i(z, t) &= i_G + i_C + i(z + \Delta z, t) \\
 &= [G \Delta z] v(z + \Delta z, t) + [C \Delta z] \frac{\partial v(z + \Delta z, t)}{\partial t} + i(z + \Delta z, t) \\
 \Rightarrow \frac{i(z + \Delta z, t) - i(z, t)}{\Delta z} &= -G v(z + \Delta z, t) - C \frac{\partial v(z + \Delta z, t)}{\partial t}
 \end{aligned}$$

9-3 General Transmission-line equations

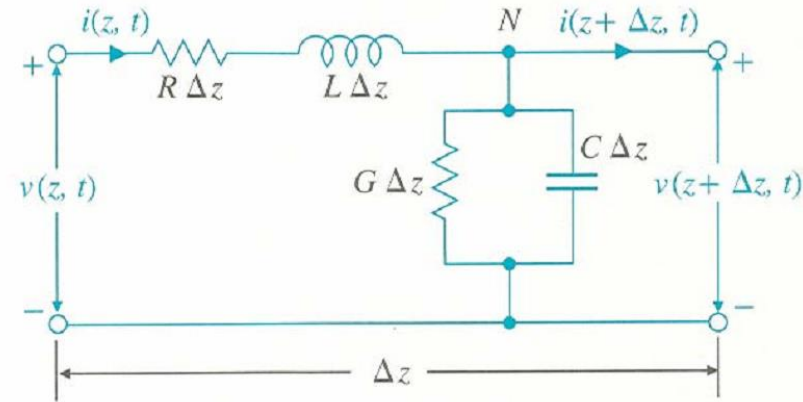2. Taking the limit as Δz tends to zero, we have



$$\frac{\partial v(z, t)}{\partial z} = -Ri(z, t) - L \frac{\partial i(z, t)}{\partial t}$$

$$\frac{\partial i(z, t)}{\partial z} = -Gv(z, t) - C \frac{\partial v(z, t)}{\partial t}$$

Time-domain form of the Transmission-line equations

Solving this equation with the appropriate initial conditions and boundary condition, we can determined the voltage and current

9-3 General Transmission-line equations

For sinusoidal steady-state conditions, phasors can be used

$$v(z, t) = \text{Re} \left[V(z) e^{j\omega t} \right]$$

$$i(z, t) = \text{Re} \left[I(z) e^{j\omega t} \right]$$

$$\begin{aligned} \frac{\partial v(z, t)}{\partial t} &= \frac{\partial \text{Re} \left[V(z) e^{j\omega t} \right]}{\partial t} & \frac{\partial v(z, t)}{\partial z} &= \frac{\partial \text{Re} \left[V(z) e^{j\omega t} \right]}{\partial z} \\ &= \text{Re} \left[V(z) \frac{\partial e^{j\omega t}}{\partial t} \right] & &= \text{Re} \left[\frac{dV(z)}{dz} e^{j\omega t} \right] \\ &= \text{Re} \left[j\omega V(z) e^{j\omega t} \right] & & \end{aligned}$$

Similarly,

$$\begin{aligned} \frac{\partial i(z, t)}{\partial t} &= \text{Re} \left[j\omega I(z) e^{j\omega t} \right] & \frac{\partial i(z, t)}{\partial z} &= \text{Re} \left[\frac{dI(z)}{dz} e^{j\omega t} \right] \end{aligned}$$

9-3 General Transmission-line equations

Therefore, the transmission-line equations becomes

$$-\frac{dV(z)}{dz} = (R + i\omega L)I(z)$$

$$-\frac{dI(z)}{dz} = (G + i\omega C)V(z)$$

- Transmission-line equations in phasor form
- The solution of the equations is the sinusoidal excited steady-state voltage and current phasor along the transmission line

9-3 General Transmission-line equations

$$-\frac{dV(z)}{dz} = (R + i\omega L)I(z) \quad -\frac{dI(z)}{dz} = (G + i\omega C)V(z)$$



$$\frac{d^2V}{dz^2} = \frac{d}{dz}(-(R + i\omega L)I) = (R + i\omega L)\left(-\frac{dI}{dz}\right) = (R + i\omega L)(G + i\omega C)V(z)$$


$$\text{let } V(z) = e^{-kz} \quad \& \quad \frac{d^2V}{dz^2} = k^2V(z)$$

$$\rightarrow \boxed{k = \alpha + i\beta = \sqrt{(R + i\omega L)(G + i\omega C)}}$$

α : attenuation constant

β : phase constant

9-3 General Transmission-line equations

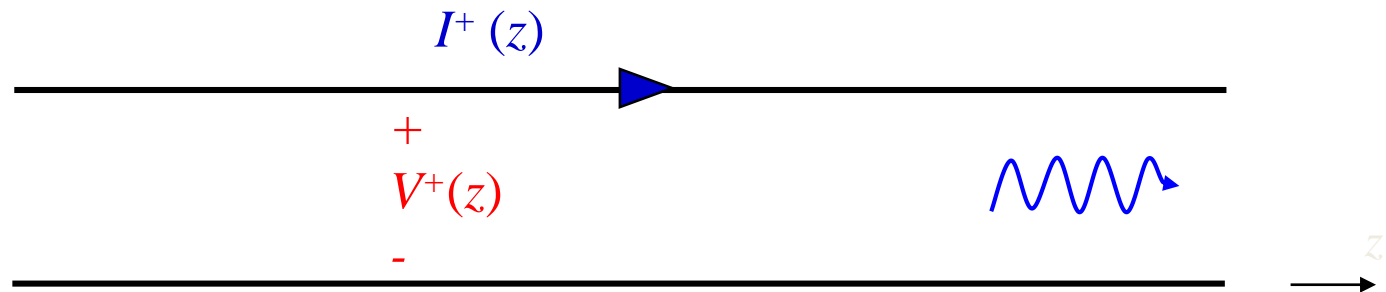

A wave is traveling in the **positive z direction**.

$$V(z) = V_0^+ e^{-kz} + V_0^- e^{+kz}$$

$$v(z, t) = V_0^+ e^{-kz + i\omega t} + V_0^- e^{+kz + i\omega t}$$

$$I(z) = I_0^+ e^{-kz} + I_0^- e^{+kz}$$

$$i(z, t) = I_0^+ e^{-kz + i\omega t} + I_0^- e^{+kz + i\omega t}$$

$$\rightarrow \frac{V_0^+}{I_0^-} = -\frac{V_0^-}{I_0^+} = \frac{R + i\omega L}{k}$$

characteristic impedance: $Z_0 = \frac{R + i\omega L}{k} = \sqrt{\frac{R + i\omega L}{G + i\omega C}} \left(\propto \frac{V/l_z}{I/l_z} \right)$

9-3 General Transmission-line equations

Three limiting cases

1. Lossless Line ($R = 0, G = 0$. There is no real part in k .)

(a) Propagation constant: $k = i\omega\sqrt{LC}$, $\alpha = 0$, $\beta = \omega\sqrt{LC}$

(b) Phase velocity: $v_{phase} = \frac{\omega}{\beta} = \frac{1}{\sqrt{LC}}$

(c) Characteristic impedance: $Z_0 = R_0 + iX_0 = \sqrt{\frac{R + i\omega L}{G + i\omega C}} = \sqrt{\frac{L}{C}}$, $R_0 = \sqrt{\frac{L}{C}}$,

$$X_0 = 0$$

9-3 General Transmission-line equations

Three limiting cases

2. Low-Loss Line ($R \ll \omega L$, $G \ll \omega C$)

(a) Propagation constant:

$$\begin{aligned} k &= i\omega\sqrt{LC} \sqrt{\left(1 - i\frac{R}{\omega L}\right)\left(1 - i\frac{G}{\omega C}\right)} \cong i\omega\sqrt{LC} \left(1 - i\frac{R}{2\omega L} - i\frac{G}{2\omega C}\right) \\ &= \frac{R}{2} \sqrt{\frac{C}{L}} + \frac{G}{2} \sqrt{\frac{L}{C}} + i\omega\sqrt{LC} \end{aligned}$$

$$\alpha \cong \frac{R}{2} \sqrt{\frac{C}{L}} + \frac{G}{2} \sqrt{\frac{L}{C}}, \quad \beta \cong \omega\sqrt{LC}$$

(b) Phase velocity: $v_{phase} = \frac{\omega}{\beta} \cong \frac{1}{\sqrt{LC}}$

(c) Characteristic impedance: $Z_0 = R_0 + iX_0 = \sqrt{\frac{R + i\omega L}{G + i\omega C}} \rightarrow$

$$Z_0 = \sqrt{\frac{L}{C}} \left(1 - i\frac{R}{\omega L}\right)^{1/2} \left(1 - i\frac{G}{\omega C}\right)^{-1/2} \cong \sqrt{\frac{L}{C}} \left(1 - i\frac{R}{2\omega L} + i\frac{G}{2\omega C}\right), \quad R_0 = \sqrt{\frac{L}{C}},$$

$$X_0 = \frac{G}{2\omega C} \sqrt{\frac{L}{C}} - \frac{R}{2\omega} \frac{1}{\sqrt{LC}}$$

9-3 General Transmission-line equations

Three limiting cases

3. Distortionless Line ($R/L = G/C$)

(a) Propagation constant: $k = i\omega\sqrt{LC}\left(1 - i\frac{R}{\omega L}\right) = \sqrt{\frac{C}{L}}R + i\omega\sqrt{LC}$

$$\alpha \cong R\sqrt{\frac{C}{L}}, \quad \beta \cong \omega\sqrt{LC}$$

(b) Phase velocity: $v_{\text{phase}} = \frac{\omega}{\beta} \cong \frac{1}{\sqrt{LC}}$

(c) Characteristic impedance: $Z_0 = R_0 + iX_0 = \sqrt{\frac{R + i\omega L}{G + i\omega C}} = \sqrt{\frac{R}{G}} = \sqrt{\frac{L}{C}} \rightarrow$

$$R_0 = \sqrt{\frac{L}{C}}, \quad X_0 = 0$$

9-3 General Transmission-line equations


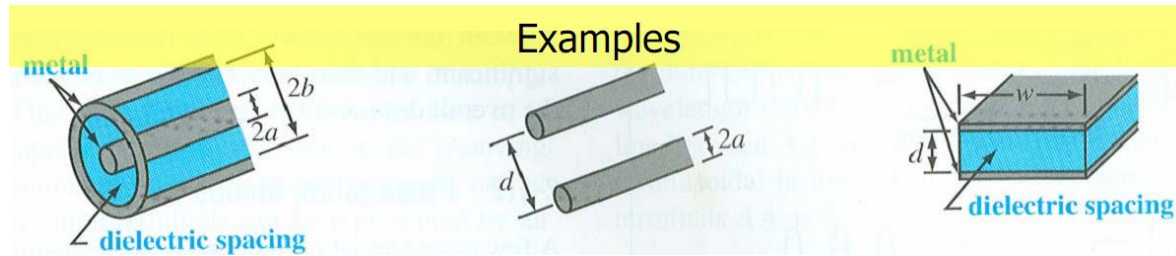


Table 2-1: Transmission-line parameters R' , L' , G' , and C' for three types of lines.

Parameter	Coaxial	Two Wire	Parallel Plate	Unit
R'	$\frac{R_s}{2\pi} \left(\frac{1}{a} + \frac{1}{b} \right)$	$\frac{R_s}{\pi a}$	$\frac{2R_s}{w}$	Ω/m
L'	$\frac{\mu}{2\pi} \ln(b/a)$	$\frac{\mu}{\pi} \ln \left[(d/2a) + \sqrt{(d/2a)^2 - 1} \right]$	$\frac{\mu d}{w}$	H/m
G'	$\frac{2\pi\sigma}{\ln(b/a)}$	$\frac{\pi\sigma}{\ln \left[(d/2a) + \sqrt{(d/2a)^2 - 1} \right]}$	$\frac{\sigma w}{d}$	S/m
C'	$\frac{2\pi\epsilon}{\ln(b/a)}$	$\frac{\pi\epsilon}{\ln \left[(d/2a) + \sqrt{(d/2a)^2 - 1} \right]}$	$\frac{\epsilon w}{d}$	F/m

Notes: (1) Refer to Fig. 2-4 for definitions of dimensions. (2) μ , ϵ , and σ pertain to the insulating material between the conductors. (3) $R_s = \sqrt{\pi f \mu_c / \sigma_c}$. (4) μ_c and σ_c pertain to the conductors. (5) If $(d/2a)^2 \gg 1$, then $\ln \left[(d/2a) + \sqrt{(d/2a)^2 - 1} \right] \simeq \ln(d/a)$.

Summary of Basic TL formulas

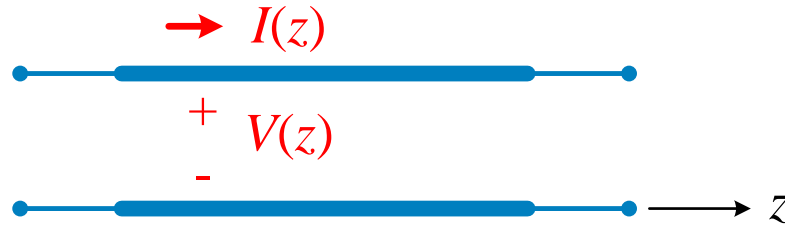

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

$$I(z) = \frac{V_0^+}{Z_0} e^{-\gamma z} - \frac{V_0^-}{Z_0} e^{+\gamma z}$$

$$\gamma = \alpha + j\beta = \left[(R + j\omega L)(G + j\omega C) \right]^{1/2}$$

$$Z_0 = \left(\frac{R + j\omega L}{G + j\omega C} \right)^{1/2}$$

guided wavelength $\equiv \lambda_g$

$$\lambda_g = \frac{2\pi}{\beta} [\text{m}]$$

phase velocity $\equiv v_p$


$$v_p = \frac{\omega}{\beta} [\text{m/s}]$$

9-4 Terminated Transmission Line

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

Ampl. of voltage wave
propagating in positive z
direction at $z = 0$.

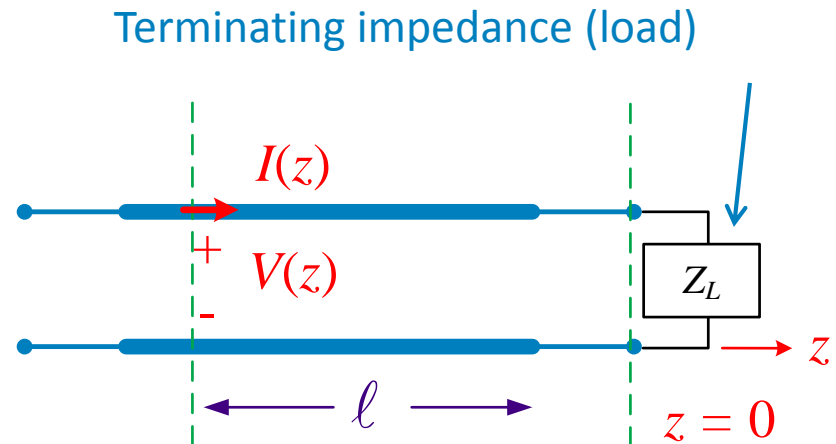Ampl. of voltage wave
propagating in negative z
direction at $z = 0$.



Where do we assign $z = 0$?

The usual choice is at the load.

Note: The length ℓ measures distance from the load: $\ell = -z$

9-4 Terminated Transmission Line

$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

What if we know

V^+ and V^- @ $z = -\ell$

Can we use $z = -\ell$ as a reference plane?


$$V_0^+ = V^+(0) = V^+(-\ell) e^{-\gamma \ell}$$

$$V^-(-\ell) = V^-(0) e^{-\gamma \ell}$$


$$\Rightarrow V_0^- = V^-(0) = V^-(-\ell) e^{\gamma \ell}$$

Hence
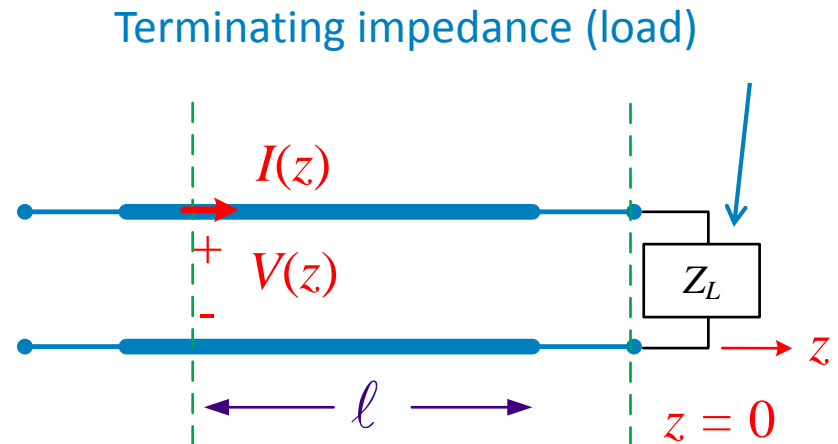
$$V(z) = V^+(-\ell) e^{-\gamma(z+\ell)} + V^-(-\ell) e^{\gamma(z+\ell)}$$



9-4 Terminated Transmission Line

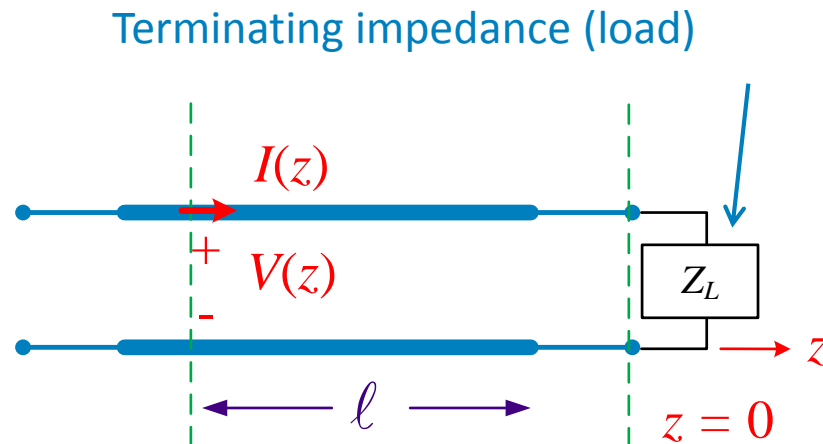

Compare:

$$V(z) = V^+(0)e^{-\gamma z} + V^-(0)e^{+\gamma z}$$

$$V(z) = V^+(-\ell)e^{-\gamma(z-(-\ell))} + V^-(-\ell)e^{\gamma(z-(-\ell))}$$

Note: This is simply a change of reference plane, from $z = 0$ to $z = -\ell$.

9-4 Terminated Transmission Line


$$V(z) = V_0^+ e^{-\gamma z} + V_0^- e^{+\gamma z}$$

What is $V(-\ell)$?

$$V(-\ell) = V_0^+ e^{\gamma \ell} + V_0^- e^{-\gamma \ell}$$

propagating forwards

propagating backwards

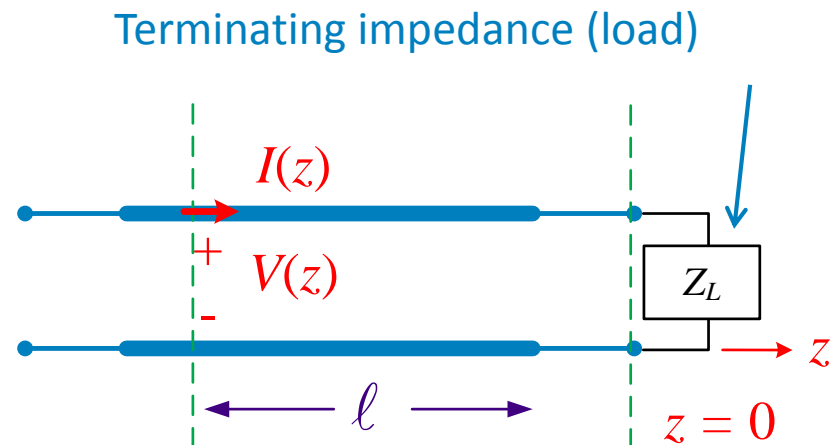


The current at $z = -\ell$ is then

$$I(-\ell) = \frac{V_0^+}{Z_0} e^{\gamma \ell} - \frac{V_0^-}{Z_0} e^{-\gamma \ell}$$

$\ell \equiv$ distance away from load

9-4 Terminated Transmission Line

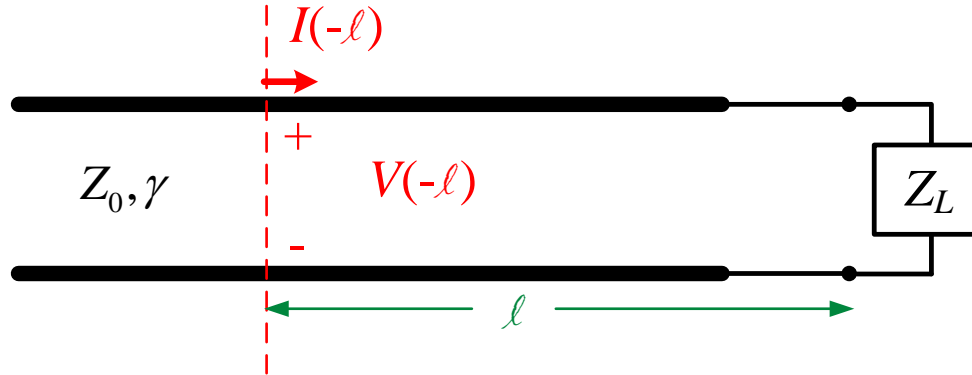

Total volt. at distance ℓ
from the load

$$V(-\ell) = V_0^+ e^{\gamma\ell} + V_0^- e^{-\gamma\ell} = V_0^+ e^{\gamma\ell} \left(1 + \frac{V_0^-}{V_0^+} e^{-2\gamma\ell} \right)$$

Ampl. of volt. wave prop.
towards load, at the load
position ($z = 0$).

Ampl. of volt. wave prop.
away from load, at the
load position ($z = 0$).

$\Gamma_L \equiv$ Load reflection coefficient


$\Gamma_\ell \equiv$ Reflection coefficient at $z = -\ell$

$$= V_0^+ e^{\gamma\ell} (1 + \Gamma_L e^{-2\gamma\ell})$$

Similarly,

$$I(-\ell) = \frac{V_0^+}{Z_0} e^{\gamma\ell} (1 - \Gamma_L e^{-2\gamma\ell})$$


9-4 Terminated Transmission Line

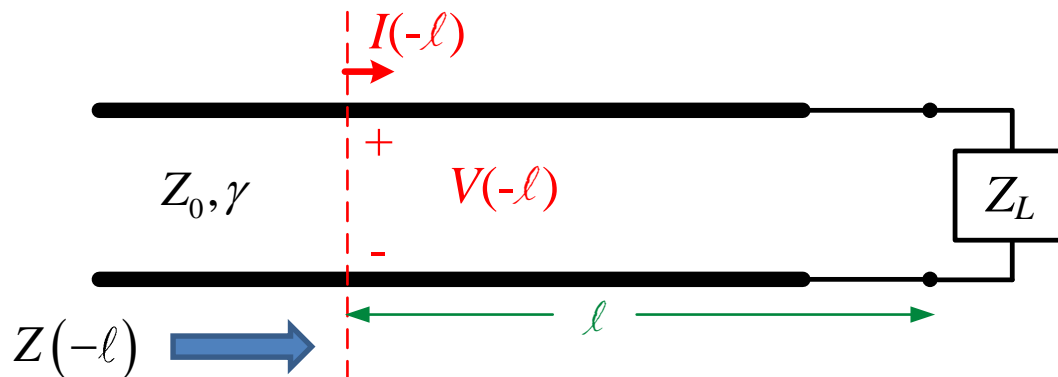

$$V(-\ell) = V_0^+ e^{\gamma \ell} (1 + \Gamma_L e^{-2\gamma \ell})$$

$$I(-\ell) = \frac{V_0^+}{Z_0} e^{\gamma \ell} (1 - \Gamma_L e^{-2\gamma \ell})$$
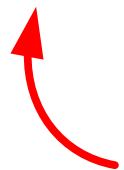
$$Z(-\ell) = \frac{V(-\ell)}{I(-\ell)} = Z_0 \left(\frac{1 + \Gamma_L e^{-2\gamma \ell}}{1 - \Gamma_L e^{-2\gamma \ell}} \right)$$



Input impedance seen “looking” towards load at $z = -\ell$.

9-4 Terminated Transmission Line

At the load ($\ell = 0$):

**Voltage reflection coefficient
of the load impedance**

$$Z(0) = Z_0 \left(\frac{1 + \Gamma_L}{1 - \Gamma_L} \right) \equiv Z_L \Rightarrow \Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma| e^{j\theta_\Gamma}$$

Recall

$$Z(-\ell) = Z_0 \left(\frac{1 + \Gamma_L e^{-2\gamma\ell}}{1 - \Gamma_L e^{-2\gamma\ell}} \right)$$

Thus,

$$Z(-\ell) = Z_0 \left(\frac{1 + \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-2\gamma\ell}}{1 - \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-2\gamma\ell}} \right)$$

9-4 Terminated Transmission Line

Simplifying, we have

$$\begin{aligned} Z(-\ell) &= Z_0 \left(\frac{1 + \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-2\gamma\ell}}{1 - \left(\frac{Z_L - Z_0}{Z_L + Z_0} \right) e^{-2\gamma\ell}} \right) = Z_0 \left(\frac{(Z_L + Z_0) + (Z_L - Z_0) e^{-2\gamma\ell}}{(Z_L + Z_0) - (Z_L - Z_0) e^{-2\gamma\ell}} \right) \\ &= Z_0 \left(\frac{(Z_L + Z_0) e^{+\gamma\ell} + (Z_L - Z_0) e^{-\gamma\ell}}{(Z_L + Z_0) e^{+\gamma\ell} - (Z_L - Z_0) e^{-\gamma\ell}} \right) \\ &= Z_0 \left(\frac{Z_L \cosh(\gamma\ell) + Z_0 \sinh(\gamma\ell)}{Z_0 \cosh(\gamma\ell) + Z_L \sinh(\gamma\ell)} \right) \end{aligned}$$

Hence, we have

$$Z(-\ell) = Z_0 \left(\frac{Z_L + Z_0 \tanh(\gamma\ell)}{Z_0 + Z_L \tanh(\gamma\ell)} \right)$$

9-4 Terminated Transmission Line

$$\gamma = \cancel{\alpha} + j\beta = j\beta$$

$$V(-\ell) = V_0^+ e^{j\beta\ell} (1 + \Gamma_L e^{-2j\beta\ell})$$

$$I(-\ell) = \frac{V_0^+}{Z_0} e^{j\beta\ell} (1 - \Gamma_L e^{-2j\beta\ell})$$

$$Z(-\ell) = Z_0 \left(\frac{1 + \Gamma_L e^{-2j\beta\ell}}{1 - \Gamma_L e^{-2j\beta\ell}} \right)$$

$$Z(-\ell) = Z_0 \left(\frac{Z_L + jZ_0 \tan(\beta\ell)}{Z_0 + jZ_L \tan(\beta\ell)} \right)$$

Impedance is periodic
with period $\lambda_g/2$

tan repeats when

$$\beta\ell = \pi$$


$$\frac{2\pi}{\lambda_g} \ell = \pi$$

$$\Rightarrow \ell = \lambda_g / 2$$

Note: $\tanh(\gamma\ell) = \tanh(j\beta\ell) = j \tan(\beta\ell)$

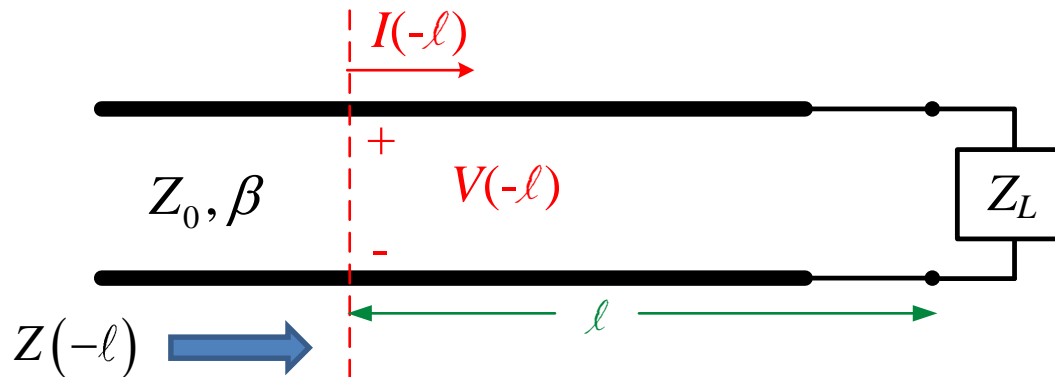9-4 Terminated Transmission Line

For the remainder of our transmission line discussion we will assume that the transmission line is lossless.



$$V(-\ell) = V_0^+ e^{j\beta\ell} (1 + \Gamma_L e^{-2j\beta\ell})$$

$$I(-\ell) = \frac{V_0^+}{Z_0} e^{j\beta\ell} (1 - \Gamma_L e^{-2j\beta\ell})$$


$$\begin{aligned} Z(-\ell) &= \frac{V(-\ell)}{I(-\ell)} = Z_0 \left(\frac{1 + \Gamma_L e^{-2j\beta\ell}}{1 - \Gamma_L e^{-2j\beta\ell}} \right) \\ &= Z_0 \left(\frac{Z_L + jZ_0 \tan(\beta\ell)}{Z_0 + jZ_L \tan(\beta\ell)} \right) \end{aligned}$$

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0}$$

$$\lambda_g = \frac{2\pi}{\beta}$$

$$v_p = \frac{\omega}{\beta}$$

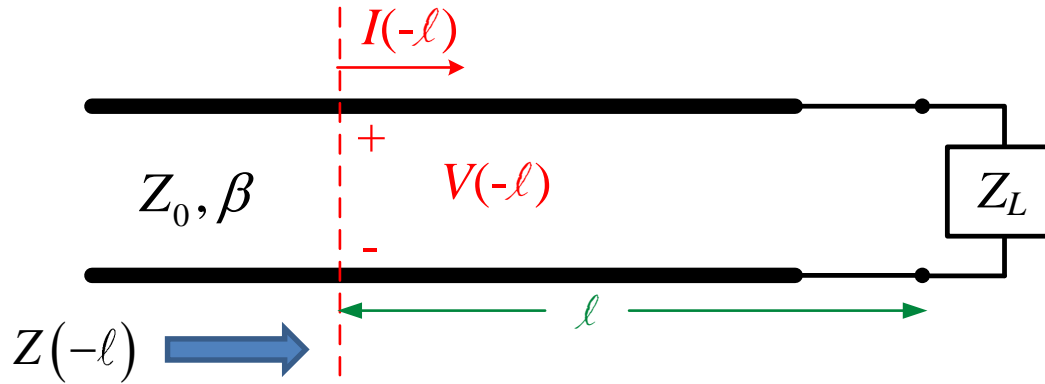9-4 Terminated Transmission Line Matched Load



(A) Matched load: ($Z_L = Z_0$)

$$\Gamma_L = \frac{Z_L - Z_0}{Z_L + Z_0} = 0$$

No reflection from the load

$$\Rightarrow V(-\ell) = V_0^+ e^{+j\beta\ell}$$

$$I(-\ell) = \frac{V_0^+}{Z_0} e^{+j\beta\ell}$$

$$\Rightarrow Z(-\ell) = Z_0$$

For any ℓ

9-4 Terminated Transmission Line

Short-Circuit Load

(B) Short circuit load: ($Z_L = 0$)

$$\Gamma_L = \frac{0 - Z_0}{0 + Z_0} = -1$$



$$\Rightarrow Z(-\ell) = jZ_0 \tan(\beta\ell)$$

Note: $\beta\ell = 2\pi \frac{\ell}{\lambda_g}$

Always imaginary!

$$\Rightarrow Z(-\ell) = jX_{sc}$$

$$X_{sc} = Z_0 \tan(\beta\ell)$$

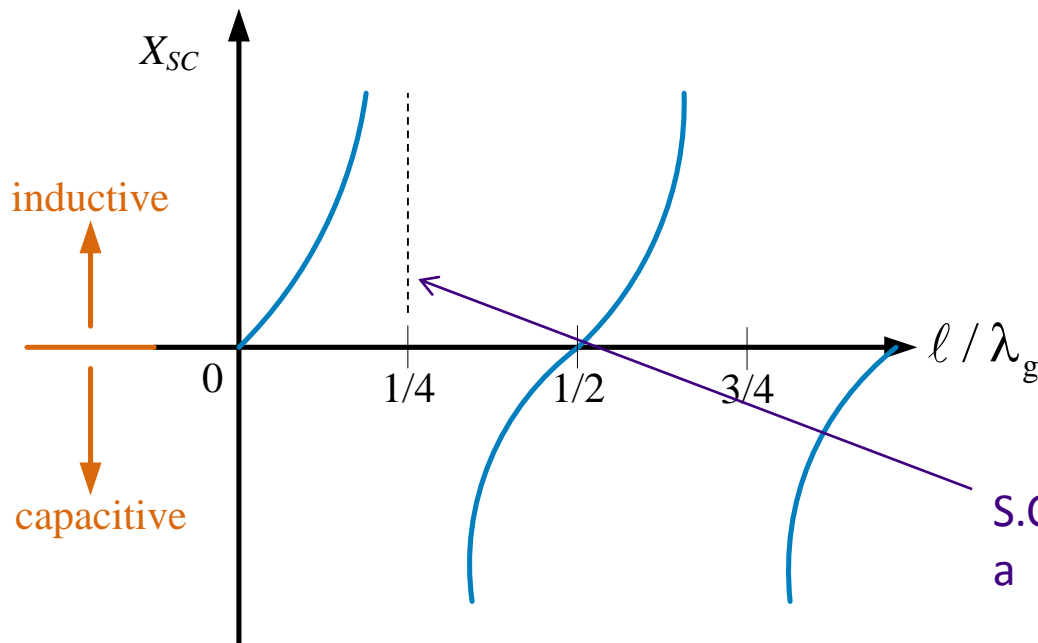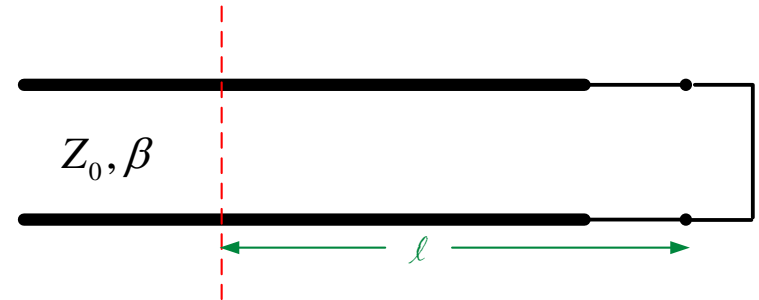

S.C. can become an O.C. with a $\lambda_g/4$ trans. line

9-4 Terminated Transmission Line

(C)

Quarter-Wave Transformer


$$Z_{in} = Z_{0T} \left(\frac{Z_L + jZ_{0T} \tan \beta \ell}{Z_{0T} + jZ_L \tan \beta \ell} \right)$$

$$\beta \ell = \beta \frac{\lambda_g}{4} = \frac{2\pi}{\lambda_g} \frac{\lambda_g}{4} = \frac{\pi}{2}$$

$$\Rightarrow Z_{in} = Z_{0T} \left(\frac{jZ_{0T}}{jZ_L} \right)$$

so

$$Z_{in} = \frac{Z_{0T}^2}{Z_L}$$

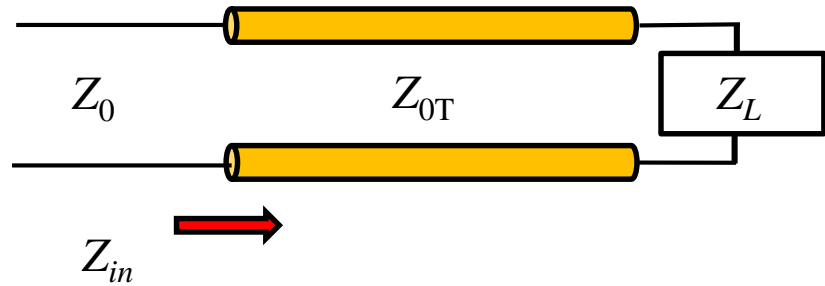

$$\Gamma_{in} = 0 \Rightarrow Z_{in} = Z_0$$

$$\Rightarrow Z_0 = \frac{Z_{0T}^2}{Z_L}$$

This requires Z_L to be real.

Hence

$$Z_{0T} = [Z_0 Z_L]^{1/2}$$

9-4 Terminated Transmission Line


Voltage Standing Wave Ratio

$$\begin{aligned} V(-\ell) &= V_0^+ e^{j\beta\ell} (1 + \Gamma_L e^{-2j\beta\ell}) \\ &= V_0^+ e^{j\beta\ell} (1 + |\Gamma_L| e^{j\phi_L} e^{-2j\beta\ell}) \end{aligned}$$

$$|V(-\ell)| = |V_0^+| |1 + |\Gamma_L| e^{j\phi_L} e^{-j2\beta\ell}|$$

$$V_{\max} = |V_0^+| (1 + |\Gamma_L|)$$

$$V_{\min} = |V_0^+| (1 - |\Gamma_L|)$$

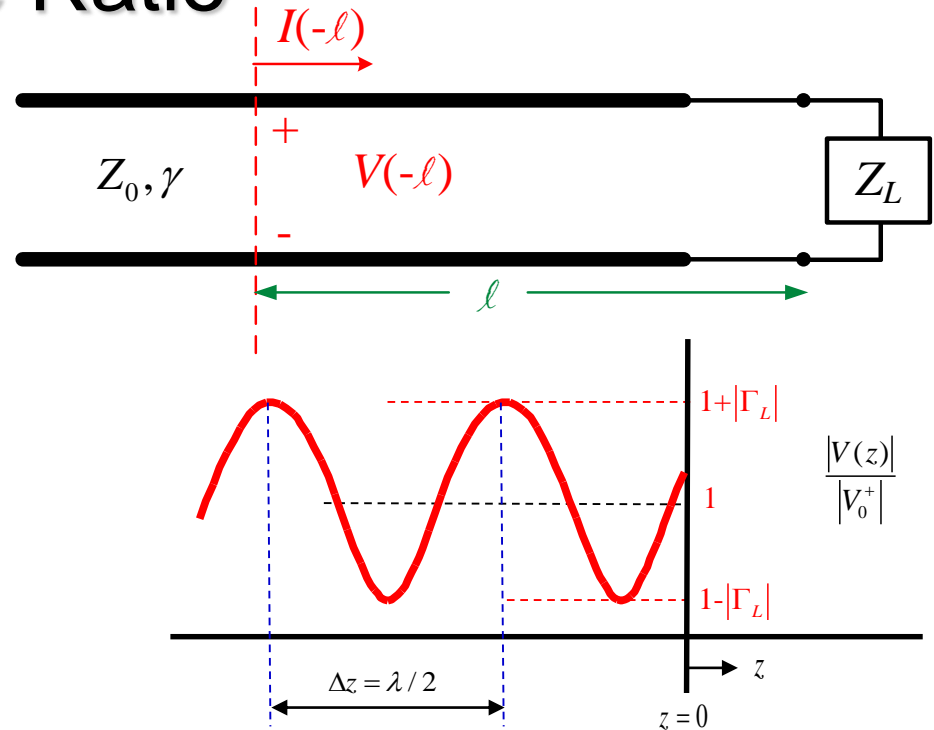

$$\text{Voltage Standing Wave Ratio (SWR)} = \frac{V_{\max}}{V_{\min}}$$

$$S = \frac{1 + |\Gamma_L|}{1 - |\Gamma_L|}$$


$\Gamma = 0$, $S = 1$ for $Z_L = Z_0$ matched load

$\Gamma = -1$, $S \rightarrow \infty$ for $Z_L = 0$ short circuit

$\Gamma = +1$, $S \rightarrow \infty$ for $Z_L \rightarrow \infty$ open circuit

9-4 Terminated Transmission Line

For resistance-terminated lossless lines

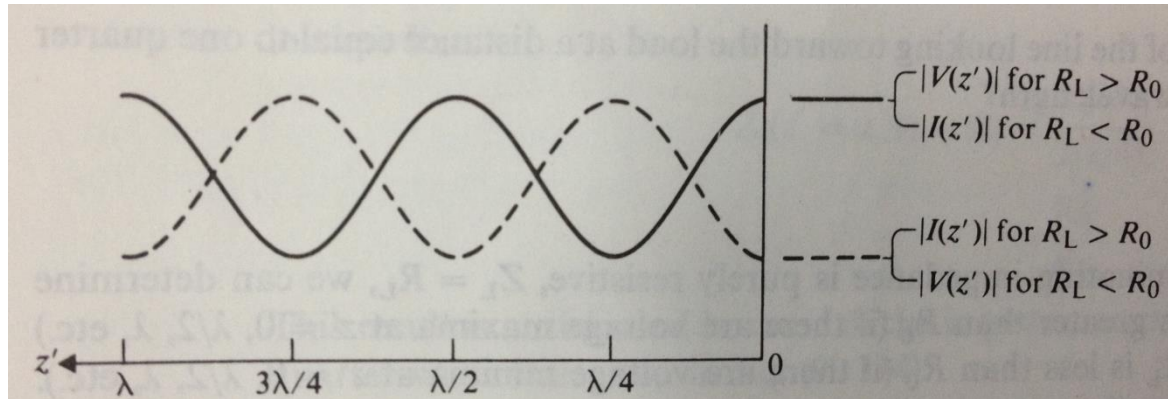

$$Z_L = R_L \quad Z_0 = R_0$$

$$R_L > R_0 \quad \theta_\Gamma = 0 \quad S = \frac{R_L}{R_0}$$


$$R_L < R_0 \quad \theta_\Gamma = -\pi \quad \frac{1}{S} = \frac{R_L}{R_0}$$

$$\Gamma = \frac{Z_L - Z_0}{Z_L + Z_0} = |\Gamma| e^{j\theta_\Gamma}$$

$$S = \frac{|V_{\max}|}{|V_{\min}|} = \frac{1 + |\Gamma|}{1 - |\Gamma|}$$

9-4 Terminated Transmission Line

Line with arbitrary termination

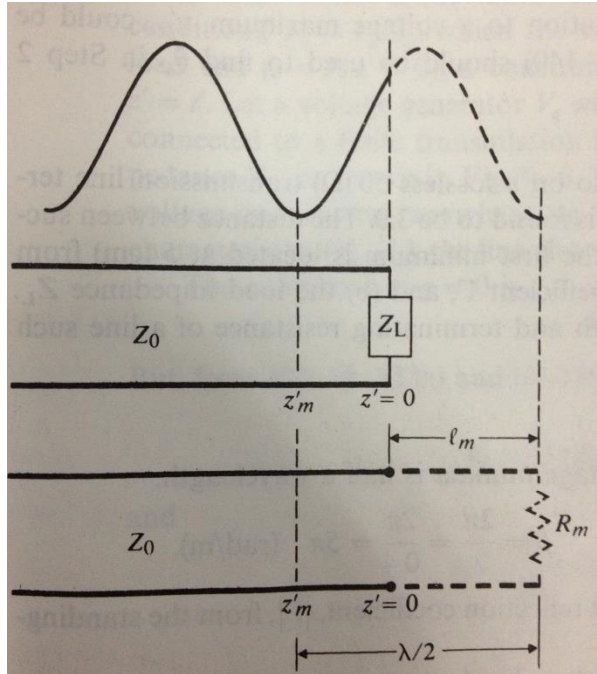

$$Z_i = R_i + jX_i = R_0 \frac{R_m + jR_0 \tan \beta l_m}{R_0 + jR_m \tan \beta l_m}$$

Z_L can be determined by measuring S and the distance z'_m

$$l_m + z'_m = \lambda/2$$

Procedure

$$|\Gamma| = \frac{S - 1}{S + 1}$$

$$\theta_\Gamma = 2\beta z'_m - \pi$$


$$Z_L = R_L + jX_L = R_0 \frac{1 + |\Gamma| e^{j\theta_\Gamma}}{1 - |\Gamma| e^{j\theta_\Gamma}}$$

9-6 Smith Chart: Introduction

Introduction

A graphical tool used to solve transmission line problems.

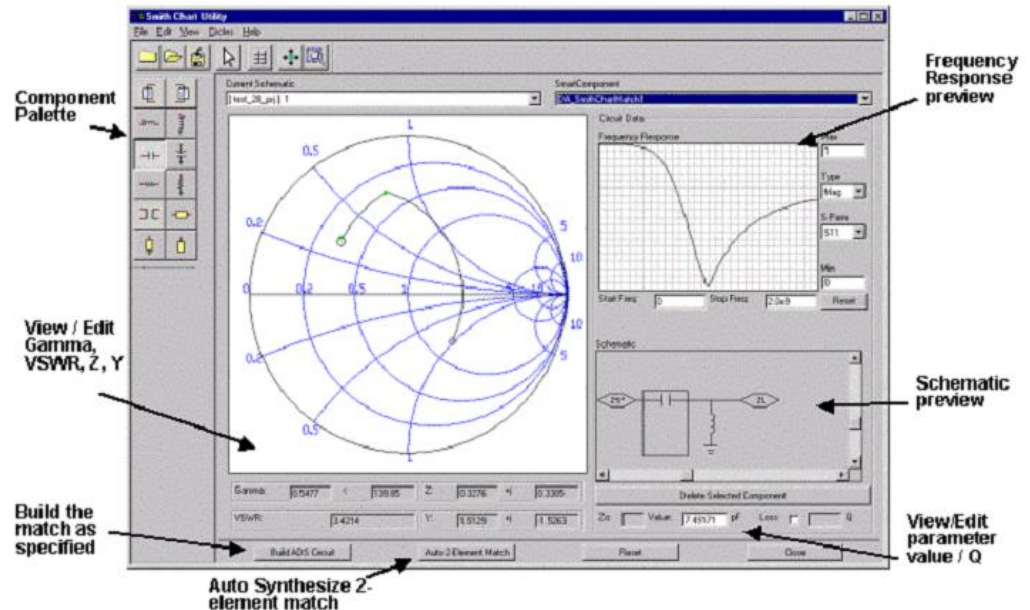Today, a presentation medium in computer-aided design (CAD) software and measuring equipment for displaying the performance of microwave circuits.



9-6 Smith-Chart


Normalized
load impedance $z_L = \frac{Z_L}{R_0} = r + jx$

Voltage reflection
coefficient $\Gamma = \frac{z_L - 1}{z_L + 1} = \Gamma_r + j\Gamma_i$

$$z_L = \frac{1 + \Gamma}{1 - \Gamma}$$

$$\left(\Gamma_r - \frac{r}{r+1}\right)^2 + \Gamma_i^2 = \left(\frac{1}{r+1}\right)^2$$
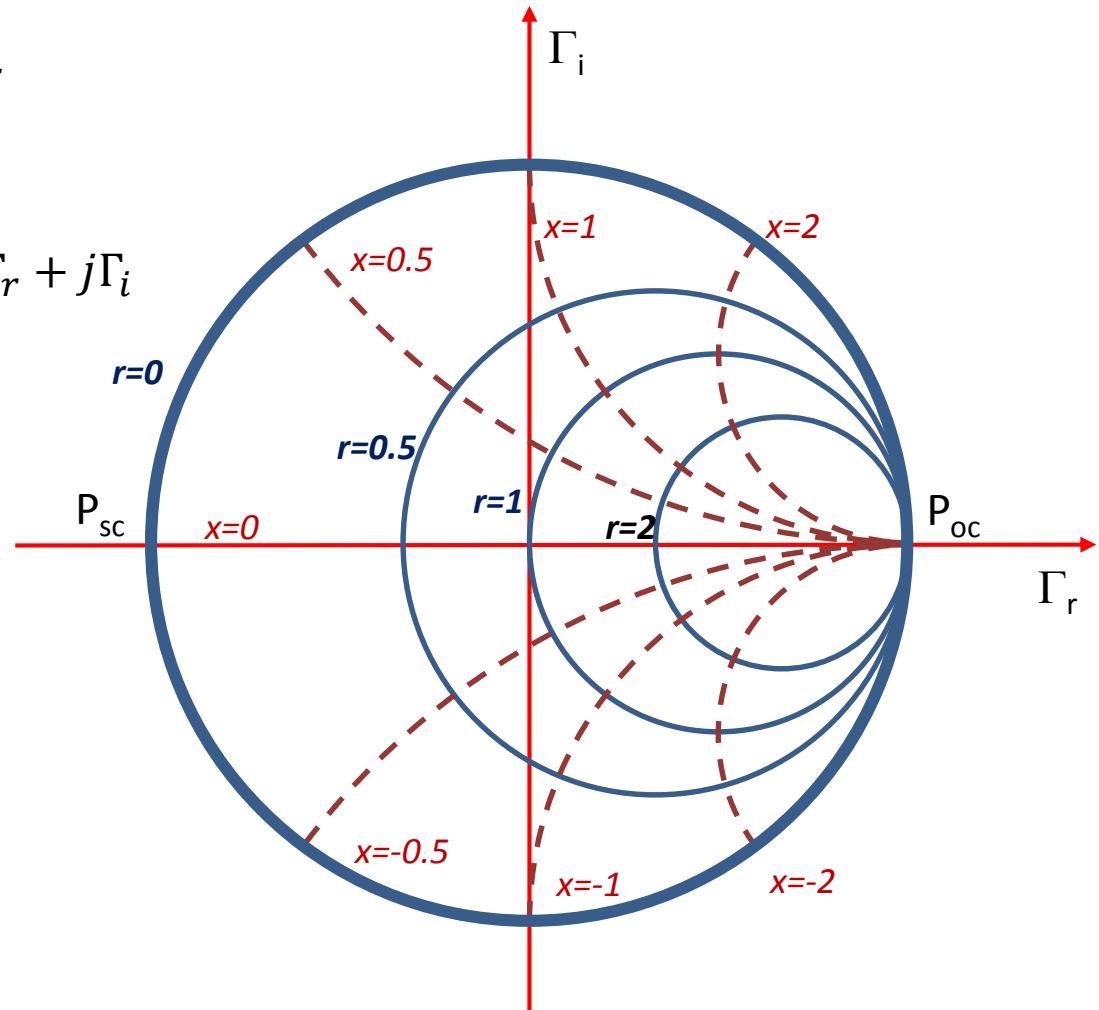
$$(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2$$



9-6 Smith-Chart


For the constant r circles:

1. The centers of all the constant r circles are on the horizontal axis – real part of the reflection coefficient.
2. The radius of circles decreases when r increases.
3. All constant r circles pass through the point $\Gamma_r = 1, \Gamma_i = 0$.
4. The normalized resistance $r = \infty$ is at the point $\Gamma_r = 1, \Gamma_i = 0$.

For the constant x (partial) circles:

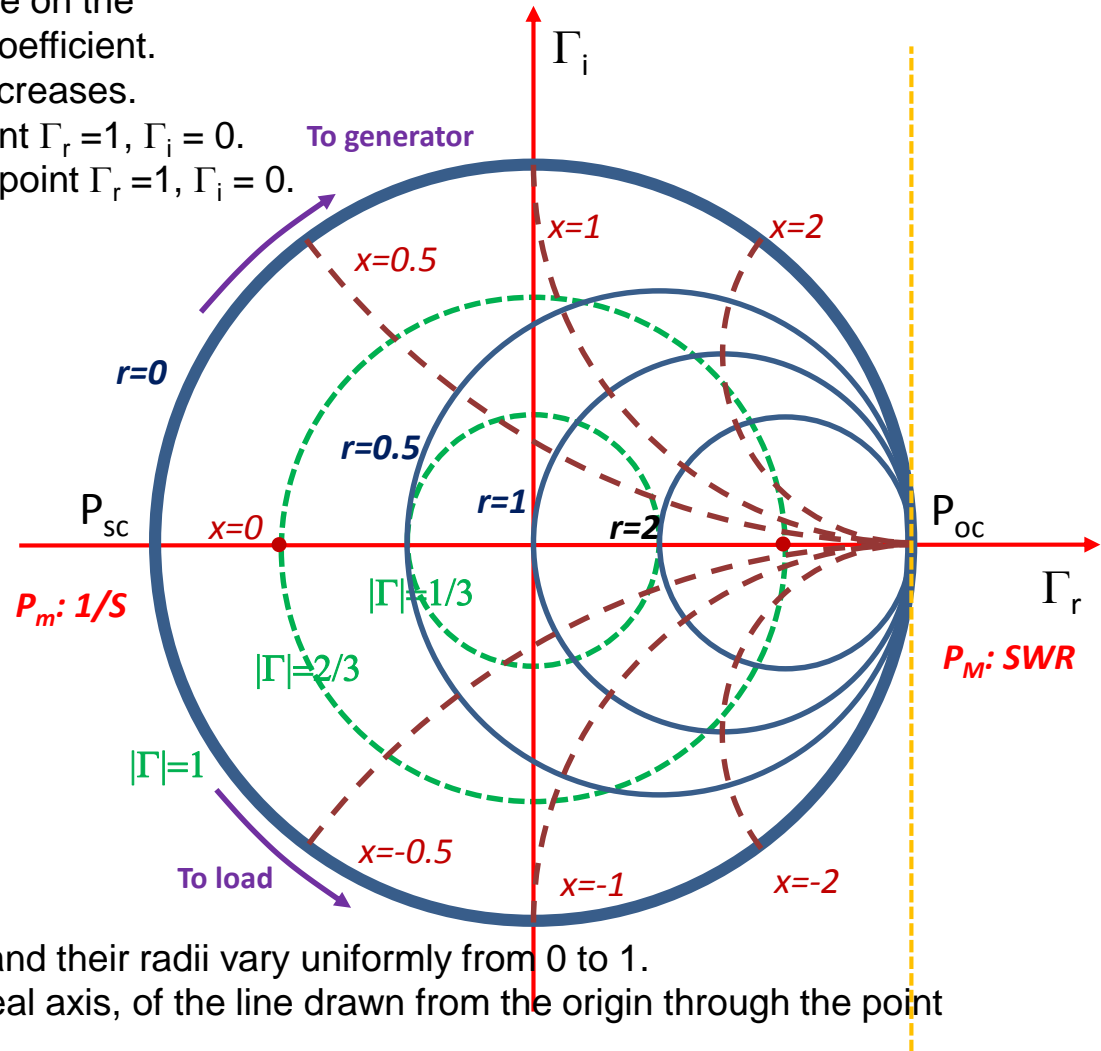
1. The centers of all the constant x circles are on the $\Gamma_r = 1$ line. The circles with $x > 0$ (inductive reactance) are above the Γ_r axis; the circles with $x < 0$ (capacitive) are below the Γ_r axis.
2. The radius of circles decreases when absolute value of x increases.
3. The normalized reactances $x = \pm\infty$ are at the point $\Gamma_r = 1, \Gamma_i = 0$

The constant r circles are orthogonal to the constant x circles at every intersection.



1. All $|\Gamma|$ -circles are centered at the origin, and their radii vary uniformly from 0 to 1.
2. The angle, measured from the positive real axis, of the line drawn from the origin through the point representing z_L equals θ_{Γ} .
3. The value of the r -circle passing through the intersection of the $|\Gamma|$ -circle and the positive real axis equals the standing-wave ratio S

Example 9-14

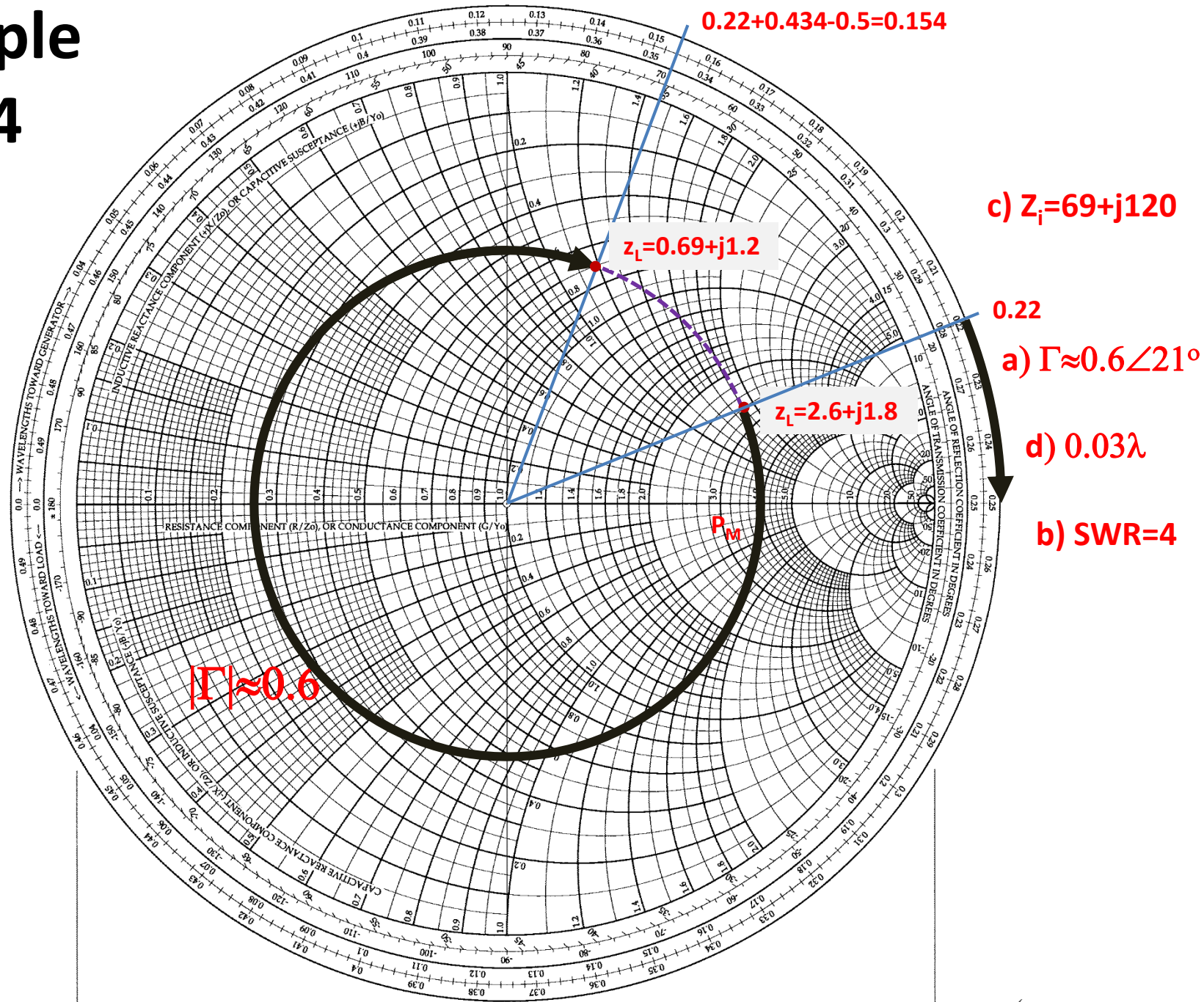


Example

9-16

$$0.364 + 0.20 - 0.5 = 0.064$$

Lossy lines

P_{sc}

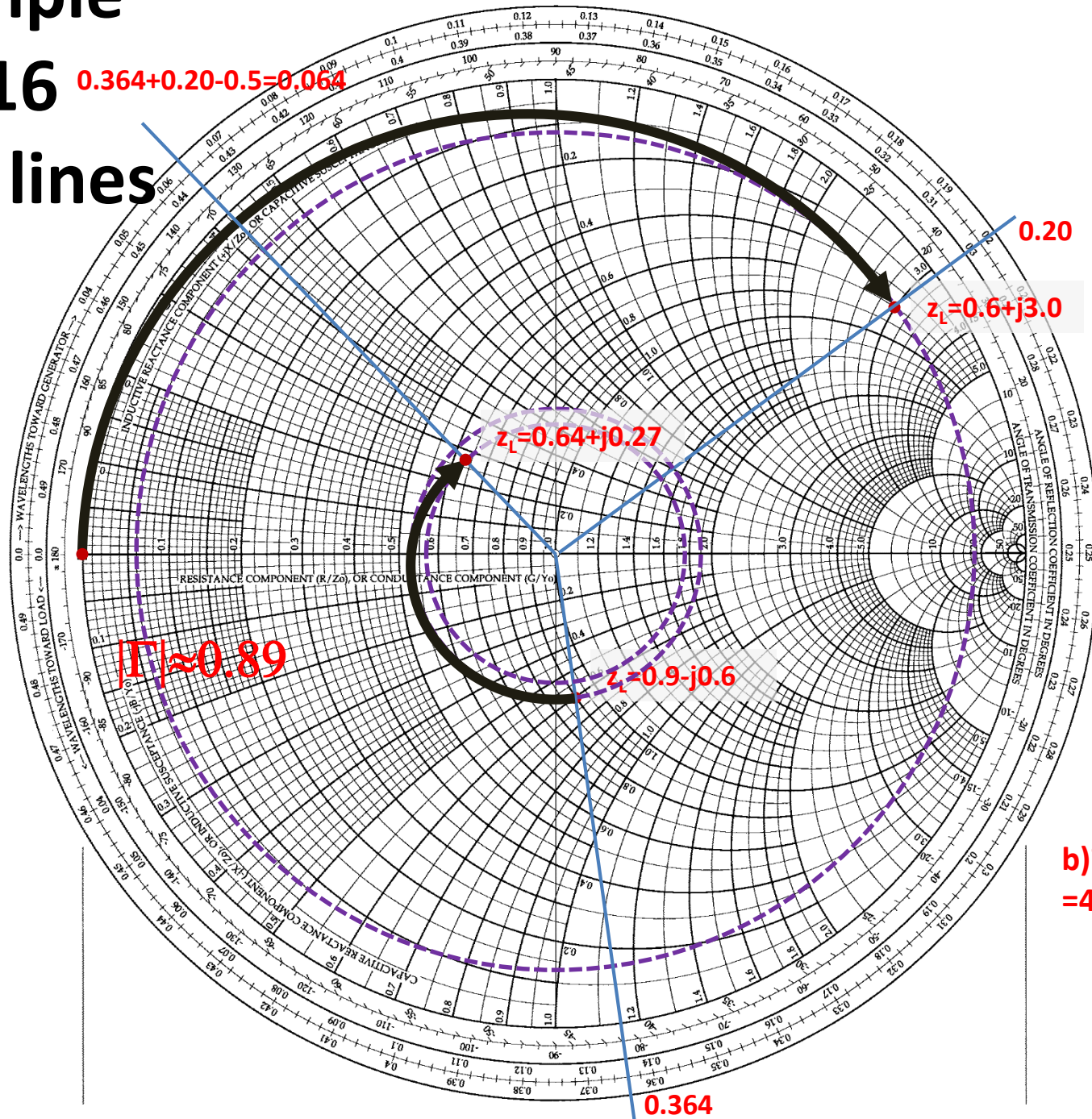

a) $\alpha = 0.029$
 $\beta = 0.2\pi$

b) $75(0.64 + j0.27)$
 $= 48.0 + j20.3$